

# Microelectronic Circuits VTU CBCS Question Paper Set 2018

VTU CAMPUS APP



Ultimate Guide to Score High In VTU Exams  
eBook ₹39/-

Guide to Score High in  
ANY VTU EXAM  
eBOOK

[Download Now](#)

USN

--	--	--	--	--	--	--	--	--	--

10EC63

**Sixth Semester B.E. Degree Examination, June/July 2013**  
**Microelectronic Circuits**

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting at least THREE from Part A and TWO from Part B.**

**PART – A**

- 1 a. Derive the equation for finite output resistance of a MOSFET. (08 Marks)
- b. For the CS-amplifier shown in Fig.Q.1(b), find  $R_{in}$ ,  $A_{v_o}$ ,  $R_{out}$  and  $G_v$  with  $r_o$  taken into account. If  $V_{sig}$  is a 0.4V (P-P) what output signal results? Assume  $R_{sig} = 10K\Omega$ ,  $R_L = 15K\Omega$ ,  $g_m = 1 \text{ mA/v}$  and  $r_o = 150K\Omega$ . (08 Marks)

 


Fig.Q.1(b)

- c. What is threshold voltage and mention its range? (04 Marks)
- 2 a. Draw the development of the T-equivalent circuit model for the MOSFET. (05 Marks)
- b. Derive the voltage gain and overall voltage equations of a source follower using MOSFET. (08 Marks)
- c. Design the circuit shown in Fig.Q.2(c) so that the transistor operates at  $I_D = 0.4 \text{ mA}$  and  $V_D = 0.5V$ . The NMOS transistor has  $V_t = 0.7V$ ,  $\mu_n C_{ox} = 100 \mu \text{ A/V}^2$ ,  $L = 1\mu\text{m}$  and  $W = 32 \mu\text{m}$ . Neglect the channel length modulation effect. (07 Marks)

 


Fig.Q.2(c)

- 3 a. What is MOSFET scaling? Mention the benefits of scaling. (06 Marks)
- b. Draw the MOSFET constant current source circuit and explain it. (06 Marks)
- c. Explain the operation of a MOS current steering circuit and mention its advantage. (08 Marks)
- 4 a. What is cascade amplifier? Explain the operation of a MOS cascade amplifier. (07 Marks)
- b. Draw the high frequency-equivalent circuit model of the MOSFET common source amplifier and explain the significance of each element. (07 Marks)
- c. Draw the three different transistor pairings and explain each configuration. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

- 5 a. Explain the operation of MOS differential pair with a differential input voltage. (07 Marks)  
b. Draw the circuit diagram of a active-loaded MOS differential pair and explain it. (08 Marks)  
c. What are the features of two-stage CMOS op-amp configuration? (05 Marks)

**PART – B**

- 6 a. Explain the effect of feedback on the amplifier poles. (06 Marks)  
b. What are the properties of negative feedbacks? Explain in detail. (08 Marks)  
c. Draw the ideal structure for the series-series feedback amplifier and explain it. (06 Marks)
- 7 a. Explain how to minimize the temperature effect in a logarithmic amplifier. (08 Marks)  
b. Draw the sample and hold circuit using op-amp and explain it. (07 Marks)  
c. Design a non-inverting op-amp with a gain of 2. At the maximum output voltage of 10V and the current in the voltage divider is to be  $10\mu\text{A}$ . (05 Marks)
- 8 a. What are the reasons for choosing CMOS over bipolar technology in digital applications? (04 Marks)  
b. Explain the dynamic operation of a CMOS inverter. (10 Marks)  
c. Implement  $F = \overline{AB + CD}$  using the AOI gate. (06 Marks)

\* \* \* \* \*

USN

--	--	--	--	--	--	--	--	--	--

10EC63

**Sixth Semester B.E. Degree Examination, June/July 2014**  
**Microelectronics Circuits**

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, selecting atleast TWO questions from each part.**

**PART – A**

1. a. With a neat diagram, derive the expression for  $i_D$  in saturation and triode region. What happened to  $i_D$  if the channel length modulation is considered? (10 Marks)
- b. Draw the large signal equivalent circuit model of NMOS and explain. (04 Marks)
- c. Determine the voltages at all nodes and the currents through all the branches of following circuit. Let  $V_t = 1V$  and  $kn'(W/L) = 1mA/V^2$ . Neglect the channel – length modulation effect. (06 Marks)

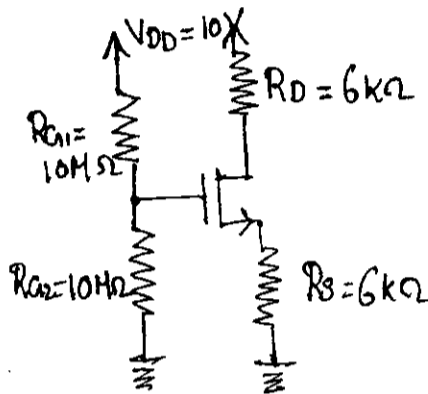


Fig.Q.1(c)

2. a. Show the development of the T equivalent – circuit model for the MOSFET from hybrid  $\pi$  model without channel length modulation. (06 Marks)
- b. Draw the circuit of common-source amplifier with a source resistance. Draw its small signal equivalent circuit with  $\gamma_0$  neglected. Obtain the expression for  $V_{gs}$ ,  $i_d$ ,  $v_o$ ,  $A_v$ ,  $A_{v0}$  and the overall voltage gain  $G_v$ . (10 Marks)
- c. What is scaling? Differentiate constant field scaling and constant-voltage scaling. (04 Marks)
3. a. Briefly explain about short channel effect due to scaling. (06 Marks)
- b. Compare NMOSFET and BJT in terms of
  - i) Current voltage characteristic.
  - ii) High frequency model.
  - iii) Output resistance. (06 Marks)
- c. Following figure shows the high frequency equivalent circuit of a common-source MOSFET amplifier. The amplifier is fed with a signal generator  $V_{sig}$  having a resistance  $R_{sig}$ . Resistance  $R$  in is due to the biasing network. Resistance  $R'_L$  is the parallel equivalent of the load resistance  $R_L$ , the drain bias resistance  $R_D$ , and the FET output resistance  $r_o$ . Capacitors  $c_{gs}$  and  $c_{gd}$  are the MOSFET internal capacitance:

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- i) Draw the equivalent circuit at midband frequencies.
- ii) Draw the circuit for determining the resistance seen by  $C_{gs}$ .
- iii) Draw the circuit for determining the resistance seen by  $C_{gd}$ . For  $R_{sig} = 100K\Omega$ ,  $R_{in} = 420K\Omega$ ,  $C_{gs} = C_{gd} = 1pF$ ,  $g_m = 4mA/V$ , and  $R'_L = 3.33K\Omega$
- iv) Find the mid band voltage gain  $A_M = V_0/V_{sig}$ .
- v) Find the upper 3-dB frequency  $f_H$ . (08 Marks)

 


Fig.Q.3(c)

- 4 a. In common-gate amplifier with active load, obtain 3-dB frequency  $f_H$  using open circuit time constants. Draw the circuit required for determining  $R_{gs}$  and  $R_{gd}$ . (08 Marks)
- b. Draw the  $C_D - C_S$ ,  $C_D - C_E$  and  $C_D - C_a$  configurations. (06 Marks)
- c. Draw an  $I_C$  source follower circuit. Obtain its small signal equivalent circuit and obtain its voltage gain  $A_v = \frac{V_0}{V_i}$ . (06 Marks)

### PART - B

- 5 a. Obtain common-gate and common-mode rejection ratio (CMRR) of the MOS differential amplifier. Also find the effect of  $R_D$  mismatch on CMRR. (12 Marks)
- b. Draw the two-stage CMOS op-amp configuration and briefly explain. Obtain overall dc open-loop gain. (08 Marks)
- 6 a. Briefly explain about
  - i) Voltage amplifier
  - ii) Current amplifier
  - iii) Trans conductance amplifier
  - iv) Trans resistance amplifier. (08 Marks)
- b. Explain about series-shunt feedback amplifier with diagram and obtain the expression for input impedance and output impedance. (08 Marks)
- c. Briefly explain about stability and pole locations. (04 Marks)
- 7 a. Draw and explain about weighted summer capable of implementing summing coefficients of both signs. (06 Marks)
- b. Explain about DC imperfections. (04 Marks)
- c. Write short notes on:
  - i) Antilogarithmic amplifiers.
  - ii) Analog multipliers. (10 Marks)
- 8 a. Draw the CMOS realization of A01 gate and explain with truth table. (08 Marks)
- b. Draw and explain the exclusive OR function using PUN and PDN. (08 Marks)
- c. What all are the parameters used to characterize the operation and performance of a logic circuit family. (04 Marks)

\* \* \* \* \*

USN

--	--	--	--	--	--	--	--	--	--

10EC63

**Sixth Semester B.E. Degree Examination, June/July 2015**  
**Microelectronics Circuits**

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE questions, selecting  
THREE from Part-A and TWO from Part-B.**

**PART – A**

1.
  - a. Derive the  $i_D - V_{DS}$  relationship of a MOSFET for triode and saturation region. (12 Marks)
  - b. For a MOSFET process technology with  $W/L = 8 \mu\text{m}/0.8 \mu\text{m}$ ,  $t_{ox} = 8\text{nm}$ ,  $\epsilon_r = 3.9$ ,  $\mu_h = 450 \text{ cm}^2/\text{v.s}$  and  $v_t = 0.7 \text{ V}$ .
    - i) Find  $C_{ox}$  and  $K'_n$ .
    - ii) Calculate the values of  $V_{GS}$  and  $V_{DSmin}$  needed to operate the transistor in the saturation region with a dc current  $I_D = 100 \mu\text{A}$ .
    - iii) For the device to operate as a  $1000 \Omega$  resistor find the value of  $V_{GS}$  required for very small  $V_{DS}$ . (08 Marks)
2.
  - a. Derive the expression for input resistance, output resistance, voltage gain and overall gain of a grounded source amplifier with a neat diagram. (08 Marks)
  - b. Design the biasing circuit shown in Fig.Q.2(b) to establish a drain current  $i_D = 0.5\text{mA}$ .

 


Fig.Q.2(b)

MOSFET has  $v_t = 1\text{V}$ ,  $k'_n(W/L) = 1 \text{ mA}/\text{v}^2$  and  $V_{DD} = 15\text{V}$ . Assume one-third  $V_{DD}$  across  $R_D$  and  $R_S$  and neglect channel length modulation  $\lambda = 0$ . Determine percentage change in value of  $i_D$  when MOSFET is replaced with another having  $v_t = 1.5\text{V}$ . (12 Marks)

3.
  - a. Explain the operation of a MOSFET current steering circuits with necessary expressions. (10 Marks)
  - b. What is MOSFET scaling? Compare MOSFET parameters before and after scaling in constant field scaling and constant voltage scaling. (10 Marks)
4.
  - a. Explain CMOS implementation of CS amplifier and arrive at voltage gain expression  $A_v = g_{m1} I_{O1}/2$ . (10 Marks)
  - b. Derive an expression for the short-circuit transconductance  $G_m$  of the MOS cascade amplifier. (10 Marks)

- 5 a. Explain operation of MOS differential pair with common-mode input voltage  $V_{cm}$  and determine the highest and lowest value of  $v_{cm}$  over which the differential pair operates properly. (08 Marks)
- b. For a MOS differential pair in Fig.Q.5(b).

 


Fig.Q.5(b)

$V_{DD} = V_{SS} = 1.5V$ ,  $k'_n(W/L) = 4mA/V^2$ ,  $v_t = 0.5V$ ,  $I = 0.4mA$ ,  $R_D = 2.5 K\Omega$  neglect channel length modulation.

- Find  $V_{OV}$  and  $V_{GS}$  for each transistor.
- What is the highest value of  $V_{an}$  for  $Q_1$  and  $Q_2$  to remain in saturation?
- If the current source  $I$  requires a minimum voltage of  $0.4V$  to operate properly what is the lowest value allowed for  $V_s$  and  $V_{an}$ ? (12 Marks)

### PART - B

- Discuss with neat diagram the four basic feedback topologies. (08 Marks)
  - Explain the properties of negative feedback. (08 Marks)
  - What is the general structure of the feedback amplifier? (04 Marks)
- Explain the operation and analysis of single op-amp difference amplifier to determine its common mode gain,  $A_{cm}$ . (10 Marks)
  - How op-amp circuits can be used as signal integrator and differentiator and determine the time constants? (10 Marks)
- Describe the circuit structure and static operation of CMOS inverter. (08 Marks)
  - With example explain PUN and PDN CMOS logic gate circuits. (08 Marks)
  - Realize two input NOR gate and two input NAND gate using CMOS gate. (04 Marks)

\*\*\*\*\*

USN

--	--	--	--	--	--	--	--	--	--

10EC63

**Sixth Semester B.E. Degree Examination, June/July 2016**  
**Microelectronic Circuits**

Time: 3 hrs.

Max. Marks: 100

**Note: Answer FIVE full questions, selecting any Three from Part-A and Two from Part-B.**

**PART – A**

- 1 a. Derive the expression of  $I_D - V_{DS}$  relationship for triode and saturation region of a NMOS transistor. (10 Marks)
- b. For the MOSFET with  $\frac{W}{L} = \frac{8 \mu\text{m}}{0.8 \mu\text{m}}$ , calculate the values of  $V_{GS}$  and  $V_{DS}(\text{min})$  needed to operate the transistor in the saturation region with a dc current  $I_D = 100$ . Assume  $K'_n = 194 \mu\text{A}/\text{V}^2$  and  $V_t = 0.7 \text{ V}$ . (05 Marks)
- c. Write the expression for the relationship between  $V_{SB}$  and  $V_t$ . Mention the effect of  $V_{SB}$  on the channel. (05 Marks)
- 2 a. What are the benefits of short channel MOSFETs? (06 Marks)
- b. Explain the operation of a MOSFET current mirror. (06 Marks)
- c. Draw the circuit of a MOS current steering circuit and explain it. (08 Marks)
- 3 a. Explain CMOS implementation of the common source amplifier and also draw its i-v characteristic of the active load and transfer characteristic. (10 Marks)
- b. Consider a common gate amplifier specified as follows :  
 $\frac{W}{L} = \frac{7.2 \mu\text{m}}{0.36 \mu\text{m}}$ ,  $\mu_n C_{ox} = 387 \mu\text{A}/\text{V}^2$ ,  $\gamma_0 = 18 \text{ K}\Omega$ ,  $I_D = 100 \mu\text{A}$ ,  $g_m = 1.25 \text{ mA}/\text{V}$ ,  $\chi = 0.2$ ,  
 $R_S = 10 \text{ K}\Omega$ ,  $R_L = 100 \text{ K}\Omega$ ,  $C_{gs} = 20 \text{ fF}$ ,  $C_{gd} = 5 \text{ fF}$  and  $C_L = 0$ . Find  $A_{VO}$ ,  $R_{in}$ ,  $R_{out}$ ,  $G_V$ ,  $G_{is}$ ,  $G_i$  and  $f_H$ . (10 Marks)
- 4 a. What is cascade amplifier? Mention the basic idea behind it. (04 Marks)
- b. Derive the expression of voltage gain and open circuit voltage gain of a IC-source follower. Draw its small signal equivalent circuit model. (08 Marks)
- c. Explain the operation of a MOS differential pair with common-mode input voltage. (08 Marks)
- 5 a. Explain the operation of a two-stage CMOS op-amp configuration. Mention its features. (10 Marks)
- b. Illustrate the method of differential to single-ended conversion. (07 Marks)
- c. What are the factors contribute to the dc offset voltage of the MOS differential pair? (03 Marks)

**PART – B**

- 6 a. Discuss the properties of negative feedback in details. (08 Marks)
- b. Explain the relationship between stability and pole location of an amplifier with effects. (06 Marks)
- c. Draw the block diagram, representation of a series-shunt feedback amplifier and derive the expression of input resistance with feedback. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.



- 7 a. Design a non-inverting amplifier with a gain of 2. At the maximum output voltage of 10 V and the current in the voltage divider is to be 10  $\mu$ A. (05 Marks)
- b. With a mathematical analysis and circuits, explain the temperature effects in Logarithmic amplifier are to be minimized. (09 Marks)
- c. Draw the sample and hold circuit using op-amp and explain it. (06 Marks)
- 8 a. Define the following parameters of a logic circuit family and write the expressions :  
i) Propagation delay.  
ii) Robustness  
iii) Delay-power product.  
iv) Dynamic power dissipation. (08 Marks)
- b. Implement :  
i)  $F = \overline{AB + CD}$  using the AND-OR-INVERT gate logic.  
ii)  $F = \overline{(A + B)(C + D)}$  using the OR-AND-INVERT gate logic. (12 Marks)

\*\*\*\*\*

USN

--	--	--	--	--	--	--	--	--	--

10EC63

**Sixth Semester B.E. Degree Examination, June/July 2017**  
**Microelectronic Circuits**

Time: 3 hrs.

Max. Marks: 100

**Note: Answer Three questions from Part A and Two from Part B.**

**PART - A**

- 1 a. Draw the  $I_D$ - $V_{DS}$  characteristics of an enhancement MOSFET. Indicate the all regions of operation and explain it. (07 Marks)
- b. For the circuit shown in Fig. Q1 (b), derive the expression of voltage gain, overall voltage gain, input impedance and output impedance. (10 Marks)

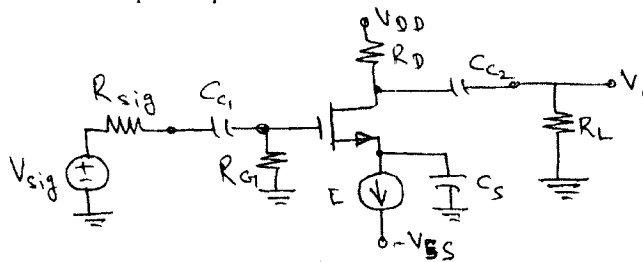


Fig. Q1 (b)

- c. An nMOS transistor has  $V_{t0} = 0.8$  V,  $2\phi_f = 0.7$  V and  $\gamma = 0.4$   $V^{1/2}$ . Find  $V_t$  when  $V_{SB} = 3$  V (03 Marks)
- 2 a. The high frequency response an amplifier is characterized by the transfer function, 
$$F_H(s) = \frac{1 - \frac{s}{10^5}}{\left(1 + \frac{s}{10^4}\right)\left(1 + \frac{s}{4 \times 10^5}\right)}$$
. Determine the 3-dB frequency. (04 Marks)
- b. Explain the operation of a current mirror using MOSFET. (08 Marks)
- c. Draw the circuit diagram to generate a number of constant currents of various magnitudes using BJT and explain it. (08 Marks)
- 3 a. Draw the circuit of a common gate amplifier with active load and explain it. (07 Marks)
- b. What is cascade amplifier? Mention the advantages of it. (04 Marks)
- c. Consider a common gate amplifier specified as follows:  $\frac{W}{L} = \frac{7.2 \mu m}{0.36 \mu m}$ ,  $\mu_n C_{OX} = 387 \mu A/V^2$ ,  $\gamma_0 = 18 K\Omega$ ,  $I_D = 100 \mu A$ ,  $g_m = 1.25$  mA/V,  $\psi = 0.2$ ,  $R_S = 10 K\Omega$ ,  $R_L = 100 K\Omega$ ,  $C_{gs} = 20$  fF,  $C_{gd} = 5$  fF and  $C_L = 0$ . Find  $A_{VO}$ ,  $R_{in}$ ,  $R_{out}$ ,  $G_v$ ,  $G_{is}$  and  $G_i$ . (09 Marks)
- 4 a. Explain the operation of a MOS cascade amplifier. (06 Marks)
- b. What is the need for transistor pairings? Draw all transistor pairings and mention advantages of each. (08 Marks)
- c. Derive the expression of CMRR of a MOS differential amplifier for the two different cases. (06 Marks)

Important Note : 1. On completing your answers compulsorily draw diagonal cross lines on the remaining blank pages.

**PART – B**

- 5 a. Explain the operation of a active loaded MOS differential pair. (08 Marks)  
 b. Why differential amplifiers are well suited for IC fabrication? (04 Marks)  
 c. With neat circuit diagram, explain the operation of two-stage CMOS op-amp circuit. (08 Marks)
- 6 a. With a mathematical analysis, explain the effect of negative feedback on gain desensitivity and bandwidth extension. (08 Marks)  
 b. Draw the structure of a series-shunt feedback amplifier and derive the expression of input and output impedance with feedback. (08 Marks)  
 c. Draw the Root locus diagram for an amplifier with three poles and explain it. (04 Marks)
- 7 a. For the circuit shown in Fig. Q7 (a), determine the values of  $V_i$ ,  $i_1$ ,  $i_2$ ,  $V_o$  and  $i_L$ . Also determine the voltage gain  $\frac{V_o}{V_i}$ , current gain  $\frac{i_L}{i_1}$  and Power gain  $\frac{P_o}{P_i}$ . (07 Marks)

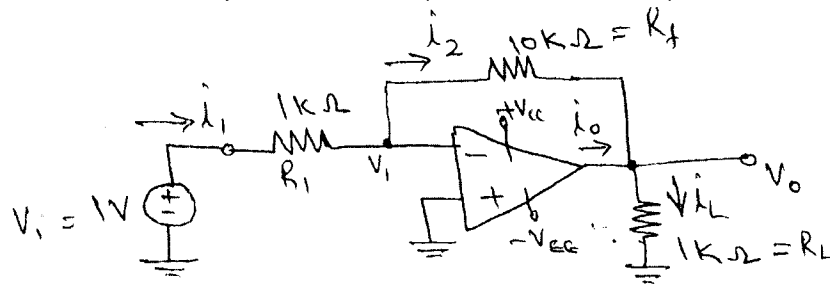


Fig. Q7 (a)

- b. Derive the output voltage expression of a logarithmic amplifier with temperature compensation. (09 Marks)  
 c. With the help of waveform, explain the effect of slew rate limiting on output sinusoidal waveform. (04 Marks)
- 8 a. Define the following performance parameter of a logic circuit family and also draw the propagation delay and switching times waveform of the logic inverter.  
 (i) Noise margin  
 (ii) Propagation delay.  
 (iii) Robustness.  
 (iv) Delay-power product. (10 Marks)
- b. Implement the following expressions using AOI gates and also write logic equivalent circuit  
 (i)  $F = \overline{(A + B)(C + D)}$   
 (ii)  $F = XY + \overline{Z}$  (10 Marks)

\* \* \* \* \*

USN

--	--	--	--	--	--	--	--	--	--

10EC63

**Sixth Semester B.E. Degree Examination, Dec.2013/Jan.2014**  
**Microelectronics Circuits**

Time: 3 hrs.

Max. Marks:100

**Note: 1. Answer FIVE full questions, selecting at least TWO questions from each part.**  
**2. State all assumptions, including missing data.**

**PART – A**

1. a. Derive an expression for drain-to-source current  $i_{DS}$  from  $i_D$  v/s  $V_{DS}$  relationship for triode and saturation regions of n-MOSFET. (10 Marks)
- b. For an  $0.8\mu\text{m}$  technology for which  $t_{OX} = 15\text{nm}$ ,  $\mu_n = 550 \text{ cm}^2/\text{V}$ . Find  $k'_n$  and  $c_{OX}$  and the overdrive voltage  $V_{ov} = V_{as} - V_t$  required to operate a transistor having  $W/L = 20$  in saturation with  $I_D = 0.2 \text{ mA}$ . What is the minimum  $V_{DS}$  needed? (06 Marks)
- c. Design the circuit shown in Fig.Q.1(c) to obtain a drain voltage of  $0.1\text{V}$ . What is the effective resistance between drain and source? At this operating point, let  $V_t = 0.8\text{V}$  and  $K'_n \left(\frac{W}{L}\right) = 1\text{mA/V}^2$ . (04 Marks)

 


Fig.Q.1(c)

2. a. Briefly explain any two types of biasing methods in MOS amplifier circuits. (06 Marks)
- b. For a common source amplifier with  $g_m = 2 \text{ mA/V}$ ,  $r_o = 50\text{K}\Omega$  and  $R_D = 10\text{K}\Omega$ ,  $R_G = 10\text{M}\Omega$ ,  $R_L = 20\text{K}\Omega$  and  $R_{sig} = 0.5\text{M}\Omega$ . Calculate  $R_{in}$ ,  $G_v$ ,  $A_v$ ,  $A_{vo}$ ,  $R_{out}$ . (10 Marks)
- c. Mention any 4 comparison of important characteristics of MOSFET and the BJT. (04 Marks)
3. a. Explain the CMOS implementation of IC common source amplifier and hence explain how to determine its small signal voltage gain. (10 Marks)
- b. For the common gate amplifier with  $W/L = 4\mu\text{m}/0.2\mu\text{m}$ ,  $\mu_n C_{OX} = 350 \mu\text{A/V}^2$ ,  $r_o = 18 \text{ K}\Omega$ ,  $I_D = 100\mu\text{A}$ ,  $g_m = 1.2 \text{ mA/V}$ ,  $\chi = 0.2$ ,  $R_s = 10\text{K}\Omega$ ,  $R_L = 100 \text{ K}\Omega$ ,  $C_{gs} = 20\text{fF}$ ,  $C_{gd} = 5\text{fF}$ ,  $C_L = 5\text{fF}$ . Find  $A_{vo}$ ,  $R_{in}$ ,  $R_{out}$ ,  $G_v$ ,  $G_{is}$ ,  $G_i$  and  $f_{H}$ . (10 Marks)
4. a. Explain the circuit of MOS cascade amplifier and hence obtain an expression for short circuit transconductance  $G_M$ . (10 Marks)
- b. Explain briefly with neat circuit diagrams:
  - i) Wilson MOS mirror (10 Marks)
  - ii) Widlar current source.

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42:8 = 50, will be treated as malpractice.

## PART - B

- 5 a. Explain the basic operation of BJT differential pair. (08 Marks)
- b. For the nMOS differential pair with a common-mode voltage  $V_{cm}$  applied as shown in Fig.Q.5(b). let  $V_{DD} = V_{SS} = 2.5V$ ,  $K'_n W/L = 3mA/V^2$ ,  $V_{th} = 0.7V$ ,  $I = 0.2mA$ ,  $R_D = 5K\Omega$ . Neglect channel length modulation.
- Find  $V_{OV}$  and  $V_{GS}$  for each transistor.
  - For  $V_{CM} = 0$  find  $V_{S1}$ ,  $i_{D1}$ ,  $i_{D2}$ ,  $V_{D1}$  and  $V_{D2}$ .
  - Repeat (ii) for  $V_{cm} = 1V$ .
  - What is the highest value of  $V_{cm}$  for which  $Q_1$  and  $Q_2$  remain in saturation, if current source  $I$  requires a minimum voltage of  $0.3V$  to operate properly. What is the lowest value for  $V_s$  and hence for  $V_{cm}$ . (12 Marks)

 


Fig.Q.5(b).

- 6 a. Explain briefly with expressions the properties of negative feedback. (08 Marks)
- b. A series-shunt feedback amplifier employs a basic amplifier with input and output resistances each of  $1K\Omega$  and gain  $A = 2000 V/V$ . The feedback factor  $\beta = 0.1 V/V$ . Find the gain  $A_f$  the input resistance  $R_i$  and output resistance  $R_o$  of the closed loop amplifier. (06 Marks)
- c. Explain briefly an alternative approach for finding loop gain  $A\beta$ . (06 Marks)
- 7 a. Explain instrumentation amplifier with neat circuit diagrams. (08 Marks)
- b. With neat diagram, explain the sample and hold circuit using opamp. (07 Marks)
- c. Derive an expression for an input resistance of the inverting amplifier taking into account the finite open loop gain  $A$  of the opamp shown in Fig.Q.7(c). (05 Marks)

 


Fig.Q.7(c)

- 8 a. Briefly discuss the parameters used to characterize the operation and performance of logic circuit families. (08 Marks)
- b. Write the expressions for propagation delay of an inverter. (05 Marks)
- c. Sketch a CMOS logic circuit that realizes the function  $Y = AB + \overline{AB}$  using equivalence or co-incidence function. (07 Marks)

\*\*\*\*\*

USN

--	--	--	--	--	--	--	--	--	--

10EC63

## Sixth Semester B.E. Degree Examination, Dec.2014/Jan.2015 Microelectronics Circuits

Time: 3 hrs.


Max. Marks:100

**Note: Answer any FIVE full questions, selecting  
atleast THREE questions from Part-A and TWO from Part-B.**

### PART – A

- 1 a. Derive an expression for drain current of a MOSFET in different regions of operation. (06 Marks)
- b. Design a circuit of Fig.Q.1(b), so that the transistor operates at  $I_D = 0.4\text{mA}$  and  $V_D = +0.5\text{V}$ . The NMOS transistor has  $V_t = 0.7\text{V}$ ,  $\mu_n C_{ox} = 100\mu\text{A/V}^2$ ,  $L = 1\mu\text{m}$ , and  $W = 32\mu\text{m}$ . Neglect channel length modulation effect ( $\lambda = 0$ ). (04 Marks)


Fig.Q.1(b)

 

- c. Draw the small signal circuit model of MOSFET when  $|V_{SB}| \neq 0$  and explain briefly. (ie including the body effect). (04 Marks)
- d. For the common drain amplifier stage, draw the small signal equivalent circuit and drive expressions for  $A_v$ ,  $A_{v0}$ ,  $G_v$ ,  $R_{in}$  and  $R_{out}$ . (06 Marks)

- 2 a. Compare and explain the important characteristics of NMOS and NPN transistors. (05 Marks)
- b. With a neat circuit diagram and equations explain the basic BJT current steering circuits. (05 Marks)
- c. For the high frequency equivalent circuit of common source amplifier in Fig.Q.2(c), find the midband voltage gain  $A_m = V_o/V_{sig}$  and upper 3dB frequency  $f_H$  using open circuit time constants. (08 Marks)


Fig.Q.2(c)

 

Where  $R_L = 3.3\text{K}\Omega$ ;  $R_{sig} = 100\text{K}\Omega$ ;  $R_{in} = 420\text{K}\Omega$ ;  $C_{gs} = C_{gd} = 1\text{pF}$ ,  $g_m = 4\text{m A/V}$ .

- d. For the emitter follower biased by a constant current source I, shown in Fig.Q.2(d), draw the high frequency equivalent circuit clearly naming all the components: (02 Marks)


Fig.Q.2(d)

 

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.


- 3 a. A CMOS common source amplifier shown in Fig.Q.3(a) is fabricated with  $W/L = 100 \mu\text{m}/1.6 \mu\text{m}$  for all transistors. With  $K_n' = 90 \mu\text{A}/\text{V}^2$ ,  $K_p' = 30 \mu\text{A}/\text{V}^2$ ,  $I_{REF} = 100 \mu\text{A}$ ,  $V_{An} = 8 \text{ V}/\mu\text{m}$  and  $V_{AP} = 12 \text{ V}/\mu\text{m}$ , determine the following quantities  $g_{m1}$ ,  $r_{o1}$ ,  $r_{o2}$ ,  $A_{vo}$ . (06 Marks)

Fig.Q.3(a)

 

- b. Draw the MOS cascade amplifier circuit with current source biasing. With the help of small signal equivalent circuit. Show that the cascading increases magnitude of open circuit voltage gain from  $A_o$  to  $A_o^2$ . (06 Marks)
- c. Write short notes on cascade MOS current mirror circuit. (04 Marks)
- d. Find  $A_o$  for an NMOS transistor fabricated in a  $0.4 \mu\text{m}$  CMOS process for which  $K_n' = 200 \mu\text{A}/\text{V}^2$ , and  $V_A' = 20 \text{ V}/\mu\text{m}$ . The transistor has a  $0.4 \mu\text{m}$  channel length and is operated with an overdrive voltage of  $0.25 \text{ V}$ . What must be  $W$  for NMOS transistor to operate at  $I_D = 100 \mu\text{A}$ ? Also find  $r_o$  and  $g_m$ . (04 Marks)
- 4 a. Explain the operation of MOS differential pair with a differential input voltage and derive the range of differential input for differential mode of operation. (08 Marks)
- b. Prove that  $A_{CM} = \frac{-r_{o4}}{2R_{SS}} \times \frac{1}{1 + g_{m3} r_{o3}}$  for the active loaded MOS differential amplifier. (08 Marks)
- c. For the BJT differential amplifier having  $\beta = 100$ , matched to 10% or better, and areas that are matched to 10% or better, along with collector resistors that are matched to 2% or better, find  $V_{OS}$ ,  $I_B$  and  $I_{OS}$ . The dc bias current is  $100 \mu\text{A}$ . (04 Marks)
- 5 a. Explain the operation of MOSFET as a linear amplifier. (05 Marks)
- b. For the common base amplifier shown in Fig.Q.5(b) draw the small signal equivalent circuit and hence derive an expression for  $R_{in}$ ,  $R_{out}$  and  $A_{vo}$ . (06 Marks)

Fig.Q.5(b)

 

- c. A MOS differential amplifier is operated at a total current of  $0.8 \text{ mA}$ , using transistors with  $W/L$  ratios of 100,  $K_n' = \mu_n C_{ox} = 0.2 \text{ mA}/\text{V}^2$ ,  $V_A = 20 \text{ V}$  and  $R_D = 5 \text{ K}\Omega$ . Find  $V_{OV} = (V_{GS} - V_t)$ ,  $g_m$ ,  $r_o$ ,  $A_d$ . (05 Marks)
- d. Explain channel length modulation effect of MOSFET. (04 Marks)

**PART – B**

- 6 a. What are the four properties of negative feed back? Briefly explain about each property. (08 Marks)
- b. For the series-shunt feedback ideal amplifier find  $A_f$ ,  $R_{if}$  and  $R_{of}$ . (06 Marks)
- c. Discuss the method of frequency compensation for modifying open loop gain  $A(s)$  so that the closed loop amplifier is stable, by introducing a new pole in transfer function at sufficiently low frequency. (06 Marks)
- 7 a. Draw the circuit diagram of basic difference amplifier and derive an expression for the output voltage  $V_{out}$  and differential input resistance  $R_{id}$ . (05 Marks)
- b. Show that the gain bandwidth product of an inverting amplifier is smaller than that of a non inverting amplifier. (05 Marks)
- c. Find the output voltage of the circuit, assuming Op. Amp M1 has DC open loop gain of  $1 \times 10^5$  and a bandwidth of 10 rad/sec., op amp M2 is an ideal op. amp (Ref.Fig.Q.7(c)). (06 Marks)

 


Fig.Q.7(c)

- d. Write a note on use of op-amp in sample and hold circuit. (04 Marks)
- 8 a. Draw the basic structure of CMOS inverter and explain the voltage transfer characteristic of CMOS inverter (08 Marks)
- b. Consider a CMOS inverter fabricated in a  $0.25\mu\text{m}$  process for which  $C_{ox} = 6\text{fF}/\mu\text{m}^2$ ,  $\mu_n C_{ox} = 115\mu\text{A}/\text{V}^2$ ,  $\mu_p C_{ox} = 30\mu\text{A}/\text{V}^2$ ,  $V_{tn} = -V_{tp} = 0.4\text{V}$  and  $V_{DD} = 2.5\text{V}$ . The W/L ratio of  $Q_N$  is  $0.375\mu\text{m}/0.25\mu\text{m}$  and for  $Q_p$  is  $1.125\mu\text{m}/0.25\mu\text{m}$ . The equivalent capacitance value is  $6.25\text{fF}$ . Find  $t_{PHL}$ ,  $t_{PLH}$  and  $t_p$ . (06 Marks)
- c. Explain with neat circuit diagrams about pull-up and pull-down networks used in CMOS logic circuits. (06 Marks)

\*\*\*\*\*





USN

--	--	--	--	--	--	--	--	--	--

10EC63

**Sixth Semester B.E. Degree Examination, Dec.2015/Jan.2016**  
**Microelectronics Circuits**

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting THREE from PART-A and TWO from PART-B.**

**PART - A**

- 1 a. Explain channel length modulation effect and derive an expression for finite output resistance of a MOSFET in saturation region. (08 Marks)
- b. Analyze the circuit shown in Fig. 1(b) to determine the voltages at all nodes and the currents through all branches let the nMOSFET  $V_t = 1V$  and  $k'_n \frac{W}{L} = 1mA/V^2$ . Assume  $\lambda = 0$ . (08 Marks)

 


Fig.Q1(b)

- c. Explain briefly biasing using constant current source. (04 Marks)
- 2 a. Derive analytical expressions for transfer characteristics of CS amplifier. (08 Marks)
- b. Fig. Q2(b) shows a discrete CS MOSFET amplifier utilizing the drain to gate feedback biasing arrangement. Determine the small signal voltage. Gain its input resistance and the largest allowable input signal. Let  $V_t = 1.5V$ ,  $k'_n \frac{W}{L} = 0.25mA/V^2$  and  $V_A = 50V$ .

 


Fig.Q2(b)

- c. Briefly explain common drain amplifier. (05 Marks)
- 3 a. With neat circuit diagram, explain basic BJT current mirror and derive an expression for CT ratio of BJT current mirror for finite  $\beta$ . (08 Marks)
- b. Derive an expression for 3dB frequency  $f_H$  for an amplifier having 2 poles and 2 zeros. (08 Marks)
- c. Explain millers theorem. (04 Marks)
- 4 a. Briefly explain common source amplifier with active load. (10 Marks)
- b. With neat circuit diagram, explain the MOS cascode amplifier. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42 : 8 = 50, will be treated as malpractice.

## PART – B

- 5 a. Explain the operation of MOS differential pair with a common mode input voltage. (07 Marks)  
 b. Briefly explain the basic operation of BJT differential pair with neat circuit diagram. (07 Marks)  
 c. Explain two stage CMOS OPAMP. (06 Marks)
- 6 a. Write a note on gain desensitivity and bandwidth extension. (06 Marks)  
 b. Draw the ideal structure and equivalent circuit of the series shunt feedback amplifier and explain. (10 Marks)  
 c. Write a note on amplifier with a single pole response. (04 Marks)
- 7 A Derive an expression for the closed load gain ( $v_o/v_i$ ) of the circuit shown in Fig. Q7(a). Assume the OPAMP is ideal. (06 Marks)

 


Fig.Q7(a)

- b. Explain instrumentation amplifier with neat circuit diagram. (08 Marks)  
 c. With neat circuit diagram, explain antilog amplifier. (06 Marks)
- 8 a. A CMOS inverter fabricated in a  $0.25 \mu\text{m}$  process has  $C_{ox} = 6 \text{ fF}/\mu\text{m}^2$ ,  $\mu_n C_{ox} = 115 \mu\text{A}/\text{V}^2$ ,  $\mu_p C_{ox} = 30 \mu\text{A}/\text{V}^2$ ,  $V_{tn} = -V_{tp} = 0.4\text{V}$  and  $V_{DD} = 2.5\text{V}$ . The W/L ratio of  $Q_n$  is  $0.375 \mu\text{m}/0.25 \mu\text{m}$ , and that for  $Q_p$  is  $1.125 \mu\text{m}/0.25 \mu\text{m}$ . The gate – source and gate drain overlap capacitances are specified to be  $0.3 \text{ fF}/\mu\text{m}$  of gate width. Further the effective value of drain body capacitances are  $C_{dbn} = 1\text{fF}$  and  $C_{dbp} = 1 \text{ fF}$ . The wiring capacitance  $C_w = 0.2\text{fF}$ . Find  $t_{PHL}$ ,  $t_{PLH}$  and  $t_p$ . (10 Marks)  
 b. Implement  $F = AB + \overline{AB}$  using AOI. (05 Marks)  
 c. Explain two single input domino CMOS gate. (05 Marks)

\*\*\*\*\*

10EC63

USN

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Sixth Semester B.E. Degree Examination, Dec.2016/Jan.2017**

**Micro Electronic Circuits**

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting at least TWO questions from each part.**

**PART - A**

- 1 a. Define the following parameters with respect to MOSFET: (05 Marks)  
i) Threshold voltage; ii) Overdrive voltage. (05 Marks)
- b. Explain the breakdown effect occurs in MOSFET. (05 Marks)
- c. Draw the biasing circuit using a drain to gate feedback resistor and explain it. (05 Marks)
- d. For the circuit shown in Fig.Q.1(d), find the values of R and  $V_D$  to obtain a current  $I_D$  of  $80\mu A$ . Let the NMOS transistor have  $V_t = 0.6V$ ,  $\mu_n C_{ox} = 200 \mu A/V^2$ ,  $L = 0.8 \mu m$  and  $W = 4 \mu m$ . Assume  $\lambda = 0$ . (05 Marks)

 


Fig.Q.1(d)

- 2 a. What are the disadvantages due to short-channel effects? (05 Marks)
- b. The high frequency response of an amplifier is characterized by the TF

$$F_H(s) = \frac{1 - \frac{s}{10^5}}{\left(1 + \frac{s}{10^4}\right) \left(1 + \frac{s}{4 \times 10^4}\right)}$$

Determine the 3-dB frequency. (05 Marks)

- c. What is current steering? Mention its advantages. (05 Marks)
  - d. Draw the circuit of basic MOSFET current source and explain it. (05 Marks)
- 3 a. Draw the circuit and small signal equivalent circuit of common source amplifier with active load and explain it. (06 Marks)
  - b. What is cascade amplifier and mention the basic idea behind the cascade amplifier? (06 Marks)
  - c. Draw the circuit of double cascading and explain it. (08 Marks)
- 4 a. Draw the transistor pairing circuits and mention the advantages of each pair. (06 Marks)
  - b. Draw the circuit of cascade MOS current mirror and explain it. (06 Marks)
  - c. Explain the operation of a MOS differential pair with a common mode input voltage and mention the relevant equations. (08 Marks)

**PART – B**

- 5 a. The differential amplifier shown in Fig.Q.5(a) uses transistors with  $\beta = 100$ . Evaluate:
- Input differential resistance ( $R_{id}$ ).
  - Overall differential voltage gain  $V_o/V_{sig}$  (neglect the effect of  $V_o$ ).
  - CMRR in dB. (Assume  $A_{cm} = 5 \times 10^{-4}$ ).
  - Input common mode resistance (assuming that the early voltage  $V_A = 100V$ . (10 Marks)

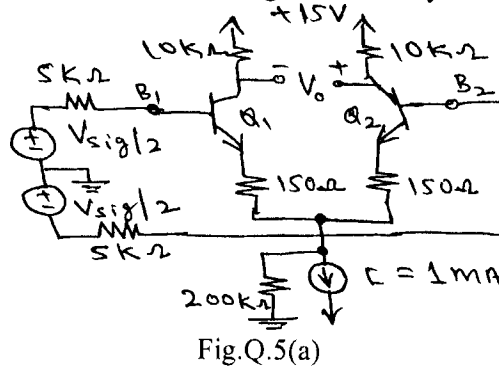


Fig.Q.5(a)

- Draw the two-stage CMOS Op-Amp circuit and explain it. (10 Marks)
- 6
- Explain the properties of negative feedback. (10 Marks)
  - Explain the effect of feedback on the amplifier stability and pole location. (07 Marks)
  - What are the properties of current amplifier? (03 Marks)
- 7 a. Derive the expression for the closed loop gain  $V_o/V_{in}$  of the circuit shown in Fig.Q.7(a). (08 Marks)

 


Fig.Q.7(a)

- With the help of mathematical analysis, explain how to minimize the temperature effect in logarithmic amplifier. (10 Marks)
  - What are DC imperfections? (02 Marks)
- 8 a. Obtain the PUN from the PDN and vice versa for the following expressions:
- $Y = \overline{A(B + CD)}$
  - $Y = \overline{\overline{A}(B + AC)}$
- (12 Marks)
- b. Define the following parameters with respect to CMOS:
- Propagation delay
  - Robustness
  - Delay power product
  - Dynamic power dissipation. (08 Marks)

USN

--	--	--	--	--	--	--	--	--	--

10EC63

**Sixth Semester B.E. Degree Examination, Dec.2017/Jan.2018**  
**Microelectronics Circuits**

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting at least TWO questions from each part.**

**PART – A**

- 1 a. What is channel length modulation? Derive the expression for finite output resistance of an NMOS transistor in saturation region. (08 Marks)
- b. Calculate the value of  $r_{DS}$  obtained for a device having  $K'_a = 100 \mu A/V^2$  and  $W/L = 10$  when operated with an overdrive voltage of 0.5V. Assume transistor is opening in triode region.
- c. Explain any three Biasing circuits in MOS amplifier. (04 Marks) (08 Marks)
- 2 a. From the small signal operation of an amplifier, derive the expression for i) DC bias point ii) Signal current in the drain terminal iii) transconductance and iv) Voltage gain. (08 Marks)
- b. A transistor amplifier is fed with a signal source having an open circuit voltage  $V_{sig}$  of 10mV and an internal resistance  $R_{sig}$  of 100k $\Omega$ .  $V_i$  and  $V_o$  are measured both without and with a load resistance  $R_L = 10k\Omega$  connected to the amplifier output. The measured result are as follows :

	$V_i$ (mv)	$V_o$ (mv)
With $R_L$	8	70
Without $R_L$	9	90

- Find: i)  $A_v$  ii)  $A_{v0}$  iii)  $G_v$  and iv)  $G_{v0}$ . (04 Marks)
- c. With a neat circuit diagram and small signal model of common drain amplifier prove that  $A_{v0} = 1$  and  $G_v = 1$ . (08 Marks)
- 3 a. For the high frequency equivalent circuit of a common source MOSFET amplifier shown in Fig. Q3(a) having  $R_{sig} = 100K\Omega$ ,  $R_{in} = 420K\Omega$ ,  $C_{gs} = C_{gd} = 1pF$ ,  $g_m = 4 MA/V$  and  $R'_L = 3.33K\Omega$ . Find the midband voltage gain  $A_m = \frac{V_o}{V_{sig}}$  and upper 3dB frequency.

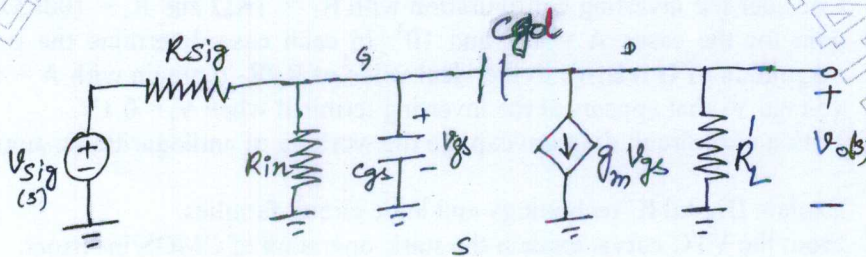


Fig Q3(a)

(08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- b. What is scaling of MOSFET? Explain two types of scaling with examples. (04 Marks)
- c. With a neat circuit diagram, explain the basic MOSFET current source and MOSFET current steering circuit. (08 Marks)
- 4 a. Derive the expression for  $R_{in}$ ,  $G_{vo}$ ,  $A_v$  and  $G_v$  of common gate amplifier with active load. (10 Marks)
- b. Consider a CC-CE amplifier such that in Fig Q4(b) with the following specifications.  $I_1 = I_2 = 1\text{mA}$ , and identical transistors with  $\beta = 100$ ,  $f_T = 400\text{MHz}$  and  $C_\mu = 2\text{pF}$ . Let the amplifier be fed with a source  $V_{sig}$  having a resistance  $R_{sig} = 4\text{K}\Omega$  and  $r_e = 25\text{m}\Omega$ . Assume a load resistance of  $4\text{K}\Omega$ ,  $g_m = 40\text{mA/V}$ . Find the voltage gain  $A_m$ . (10 Marks)

 


Fig Q 4(b)

**PART - B**

- 5 a. Derive the expression for common mode gain common mode rejection ratio of the MOS Differential amplifier. (10 Marks)
- b. With a neat circuit diagrams explain the working of active loaded MOS Differential pair. (10 Marks)
- 6 a. With a neat block diagram, explain the General structure of feedback. (08 Marks)
- b. Explain the effect of phase margin on closed loop response and hence prove that  $|A_r(j\omega_1)| = \frac{1.3}{\beta}$ . (04 Marks)
- c. Explain the properties of Negative feedback. (08 Marks)
- 7 a. With neat circuit diagram, explain the working of instrumentation amplifier. (08 Marks)
- b. Consider the inverting configuration with  $R_1 = 1\text{K}\Omega$  and  $R_2 = 100\text{K}\Omega$ . Find the closed loop gain for the cases  $A = 10^3$  and  $10^4$ . In each case determine the percentage error in the magnitude of  $G$  relative to the ideal value of  $R_2/R_1$  (contain with  $A = \infty$ ) Also determine the voltage  $V_1$  that appears at the inverting terminal when  $V_i = 0.1\text{V}$ . (06 Marks)
- c. With a neat circuit diagram explain the working of antilogarithmic amplifier. (06 Marks)
- 8 a. Explain Digital IC technology and logic circuit families. (08 Marks)
- b. From the VTC curve, explain the static operation of CMOS invertors. (06 Marks)
- c. With example explain the working of CMOS logic gate circuit. (06 Marks)

\*\*\*\*\*