

# Basic Electronics VTU CBCS Question Paper Set 2018



Ultimate Guide to Score High In VTU Exams  
eBook ₹39/-

Guide to Score High in  
ANY VTU EXAM  
eBOOK

[Download Now](#)

# CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

17ELN15

## First Semester B.E. Degree Examination, Dec.2017/Jan.2018

### Basic Electronics

Max. Marks: 100

Time: 3 hrs.

Note: Answer any FIVE full questions, choosing one full question from each module.

#### Module-1

- 1 a. Explain the operation of PN junction diode under forward and reverse biased conditions, with the help of VI characteristics curve. (06 Marks)
- b. Derive the relation between  $\alpha$  and  $\beta$ . Calculate  $I_C$  and  $I_E$  for transistor that has  $\alpha_{dc} = 0.98$  and  $I_B = 100 \mu A$ . (06 Marks)
- c. With a neat circuit diagram and waveforms, explain the working of centre-tap full wave rectifier and derive the efficiency for the same. (08 Marks)

OR

- 2 a. With a neat diagram, explain the operation of PNP and NPN transistor. (08 Marks)
- b. A half wave rectifier from a supply 230 V 50 Hz with step down transformer ratio 3:1 to a resistive load of 10 K $\Omega$ . The diode forward resistance is 75  $\Omega$  and transformer secondary is 10  $\Omega$ . Calculate the DC current, DC voltage, efficiency and ripple factor. (06 Marks)
- c. With neat circuit diagram, explain the common emitter circuit and sketch the input and output characteristics. (06 Marks)

#### Module-2

- 3 a. With a necessary equation and circuit, explain the base-bias transistor circuits. (06 Marks)
- b. Design an Adder using op-amp to give the output voltage,  $V_0 = -[2V_1 + 3V_2 + 5V_3]$  (06 Marks)
- c. Derive the equations for output voltage for an inverting amplifier and an integrator. (08 Marks)

OR

- 4 a. Explain the characteristics of an ideal op-amp. Mention the applications. (06 Marks)
- b. Accurately analyze the voltage divider bias which has  $V_{CC} = 18 V$ ,  $R_1 = 33 K\Omega$ ,  $R_2 = 12 K\Omega$  and  $R_E = 1 K\Omega$ . Determine  $V_E$ ,  $V_C$ ,  $V_{CE}$ ,  $I_C$  and Q point, when transistor  $h_{fe} = 200$ . (08 Marks)
- c. Write short notes on op-amp virtual ground concept. (06 Marks)

#### Module-3

- 5 a. Perform the following:
  - i) Convert  $(57345)_{10} = ( )_{16}$  (06 Marks)
  - ii) Subtract  $(28)_{10} - (19)_{10}$  using 2's complement method. (06 Marks)
- b. Realize  $Y = AB + CD + E$  using NAND gate. (06 Marks)
- c. Explain the full adder circuit with truth table. Realize the circuit for sum and carry using logic gates. (08 Marks)

OR

- 6 a. Perform the following:
- Convert  $(FA27D)_{16} = ( )_2 \rightarrow = ( )_8 = ( )_{10}$
  - Subtract  $10.0101 - 101.1110$  using 1's complement method. (06 Marks)
- b.  $Y = A + AB + ABC$  simplify and implement using logic gates and NOR gates. (06 Marks)
- c. State and prove De Morgan's theorem using two variable. (08 Marks)

**Module-4**

- 7 a. Bring out differences between flip flops and latches. (04 Marks)
- b. Explain SR flipflop with circuit diagram and truth table. (06 Marks)
- c. With a neat block diagram explain the architecture of 8051 microcontroller. (10 Marks)

OR

- 8 a. Explain the operation of NAND gate latch with circuit and truth table. (10 Marks)
- b. What is stepper motor? With a neat block diagram, explain the working principle of microcontroller based stepper motor control system. (10 Marks)

**Module-5**

- 9 a. Define communication. With neat block diagram, explain the elements of communication system. (06 Marks)
- b. Derive an expression for amplitude modulation and draw the necessary waveforms. (08 Marks)
- c. What is transducer? Compare the active and passive transducers. (06 Marks)

OR

- 10 a. Bring out the difference between amplitude modulation and frequency modulation. (06 Marks)
- b. If a FM wave represented by the equation  $V = 10\sin(8 \times 10^8 + 4\sin 1000t)$ , calculate:
- Carrier frequency
  - Modulating frequency
  - Modulation index
  - Band width
- (06 Marks)
- c. With necessary diagram and equations, explain the following:
- Piezo-electric transducer
  - LVDT.
- (08 Marks)

\* \* \* \* \*

# CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

15ELN15/25

## First/Second Semester B.E. Degree Examination, Dec.2016/Jan.2017 Basic Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer FIVE full questions, choosing one full question from each module.

### Module-1

- 1 a. Define the following diode parameters : (05 Marks)
  - i) Knee voltage
  - ii) Maximum forward current
  - iii) Peak inverse voltage
  - iv) Reverse breakdown voltage
  - v) Maximum power rating. (06 Marks)
- b. With neat circuit diagram and waveform explain the working of Full wave Bridge Rectifier. (06 Marks)
- c. Draw common emitter circuit. Sketch input and output characteristics. Also explain operating regions by indicating them on characteristic curve. (05 Marks)

OR

- 2 a. Write a note on voltage regulator circuit. (05 Marks)
- b. Derive the relationship between  $\alpha$  and  $\beta$ . Also calculate the  $\alpha$  value and  $\beta$  value of a transistor if  $I_B = 100\mu A$  and  $I_C = 2mA$ . (04 Marks)
- c. With a neat diagram, explain the output characteristics of a transistor in common base configuration. (07 Marks)

### Module-2

- 3 a. What is DC load line? Explain with neat circuit the operation of voltage divider bias circuit. (05 Marks)
- b. What is op-amp? List the characteristics of an ideal op-amp. (06 Marks)
- c. For the circuit shown in Fig Q3(c). compute
  - i) Three transistor currents
  - ii) Voltage drop across  $R_C$  and  $R_B$ . (05 Marks)

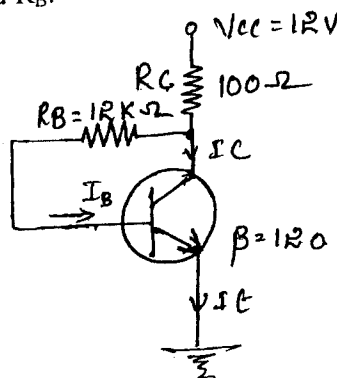


Fig Q3(b)

OR

- 4 a. Explain how op-amp can be used as  
 i) An integrator ii) Differentiator iii) Voltage follower. (06 Marks)  
 b. With neat circuit diagram, explain base biased method with necessary equations. (05 Marks)  
 c. Find the output of the following op-amp circuit. (05 Marks)

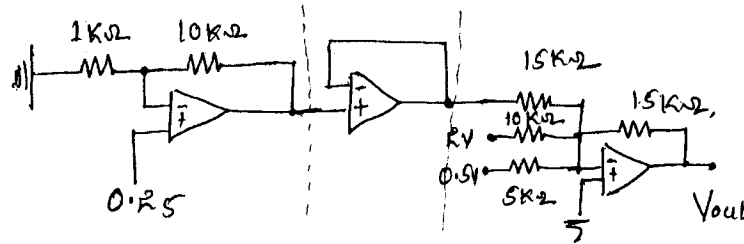


Fig Q4(c)

Module-3

- 5 a. Convert  $(1101101)_2 = ( )_{10}$  and  $(96)_{10} = ( )_2$ . (04 Marks)  
 b. Convert  $(FA876)_{16} = ( )_8$  and  $(237)_8 = ( )_{16}$ . (04 Marks)  
 c. Design Full adder circuit. (08 Marks)

OR

- 6 a. State and prove De Morgan's theorem. (05 Marks)  
 b. What are Universal gates? Realize AND, OR Gates using Universal gates. (05 Marks)  
 c. Subtract  $(19)_{10}$  from  $(15)_{10}$  using 1s and 2s complement methods. (06 Marks)

Module-4

- 7 a. Write a note on NOR gate latch. (05 Marks)  
 b. Explain the working of clocked RS flip flop using NAND gates. (06 Marks)  
 c. Define microcontrollers. Write their important applications. (05 Marks)

OR

- 8 a. Explain the architecture of 8051 micro controller. (08 Marks)  
 b. Mention the difference between latch and Flip flop. (02 Marks)  
 c. Write a note on interfacing of 8051 microcontroller with stepper motor. (06 Marks)

Module-5

- 9 a. Explain the block diagram of communication system. (05 Marks)  
 b. Define Amplitude modulation. Derive mathematical expression for the same. Draw waveforms. (06 Marks)  
 c. Explain the construction and the principle of operation of LVDT. (05 Marks)

OR

- 10 a. List the differences between Amplitude modulation and frequency modulation. (05 Marks)  
 b. Explain frequency modulation with neat waveforms. (05 Marks)  
 c. A carrier of 10V peak and frequency 100KHz is amplitude modulated by a sine wave of 4V peak and frequency 1000Hz. Determine the modulation index for the modulated wave and draw the amplitude spectrum. (06 Marks)

\* \* \* \* \*

# CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

15ELN15/25

First/Second Semester B.E. Degree Examination, Dec.2017/Jan.2018

## Basic Electronics

Max. Marks: 80

Time: 3 hrs.

Note: Answer any FIVE full questions, choosing one full question from each module.

### Module-1

- 1 a. Explain the V-I characteristics of p-n junction diode. (05 Marks)
- b. The input voltage applied to the primary of a 4:1 step down transformer of a full wave centre tap rectifier is 230 V, 50 Hz is the load resistance is 600  $\Omega$  and forward resistance is 20  $\Omega$ . Determine the following for circuit shown in Fig.Q1(b).
  - i) dc power output
  - ii) Rectification efficiency
  - iii) PIV

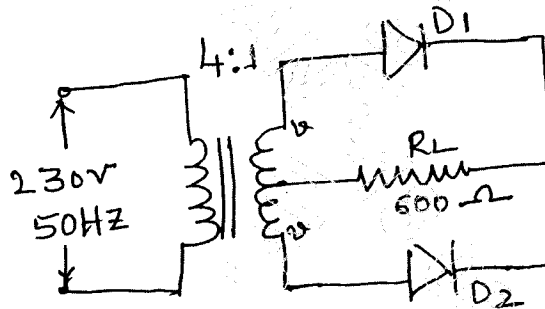


Fig.Q1(b)

- c. Explain CB configuration of BJT with characteristics. (06 Marks)

OR

- 2 a. Derive an expression for ripple factor and output dc voltage of a full wave rectifier. (06 Marks)
- b. Explain how a zener diode can be used as a voltage regulator. (05 Marks)
- c. Obtain the relationship between  $\alpha$  and  $\beta$ . Calculate the value of  $I_C$ ,  $I_E$  for a transistor that has  $\alpha = 0.98$  and  $I_B = 100 \mu A$ . (05 Marks)

### Module-2

- 3 a. What is DC load line? Explain collector to base biased method with necessary equation. (05 Marks)
- b. Define the following terms with respect to op-amp: (i) Slew rate, (ii) CMRR, (iii) PSRR. (05 Marks)
- c. Design an op-amp circuit that will produce an output equal to  $-(4V_1 + V_2 + 0.1V_3)$ . (06 Marks)

OR

- 4 a. With circuit diagram, explain the operation of voltage divider bias circuit with necessary equations. (06 Marks)
- b. Derive the expression of 3-i/p summing amplifier. (05 Marks)
- c. Draw the circuit of inverting op-amp. Derive the expression for the voltage gain. (05 Marks)

**Module-3**

- 5 a. Perform the following:
- Convert  $(725.25)_{10} = ( ? )_{10} = ( ? )_2$
  - Subtract using 2's complement  $(4 - 9)_{10}$
  - $(11010.101)_2 = ( ? )_8 = ( ? )_{16}$  (06 Marks)
- b. State and prove Demorgan's theorem. (05 Marks)
- c. Simplify the expression and realize using basic gates  $\overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + A\overline{B}C$ . (05 Marks)

**OR**

- 6 a. Convert:
- $(172.625)_{10} = ( ? )_{16} = ( ? )_2$
  - $(BDCE)_{16} = ( ? )_2 = ( ? )_8$
  - $(10111101.0110)_2 = ( ? )_{10} = ( ? )_{16}$  (06 Marks)
- b. Simplify and realize the Boolean expression using two inputs NAND gates only  $(A + \overline{B} + C)(\overline{A} + B + C)$ . (05 Marks)
- c. Realize the full adder circuit for sum and carry using basic gates, explain the same with truth table. (05 Marks)

**Module-4**

- 7 a. Explain the operation of NAND and NOR latch with symbol, circuit and truth table. (08 Marks)
- b. With neat block diagram, describe the architecture of 8051 microcontroller. (08 Marks)

**OR**

- 8 a. What is flip-flop? Explain clocked R-S flip-flop with diagram and truth table. (08 Marks)
- b. Explain the working principle of microcontroller based stepper motor control system. (08 Marks)

**Module-5**

- 9 a. What are the basic elements of communication system? Explain with neat block diagram. (06 Marks)
- b. Distinguish between Amplitude Modulation (AM) and Frequency Modulation (FM). (04 Marks)
- c. Explain the construction and the principle of operation of LVDT. (06 Marks)

**OR**

- 10 a. With relevant waveforms, explain amplitude modulation. (06 Marks)
- b. What is a transducer? Mention four important parameters of an electrical transducer. (04 Marks)
- c. Write short notes on:
- Piezo electric transducer
  - Photo electric transducer. (06 Marks)

\* \* \* \* \*

# CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

15ELN15/25

## First/Second Semester B.E. Degree Examination, June/July 2016 Basic Electronics

Time: 3 hrs.


Max. Marks: 80

**Note:** Answer any FIVE full questions, choosing one full question from each module.

### Module-1

- 1 a. Explain the operation of pn junction diode under forward and reverse bias condition. (06 Marks)
- b. For a zener regulator shown in the Fig.Q.1(b), calculate the range of input voltage for which output will remain constant.

Fig.Q.1(b)

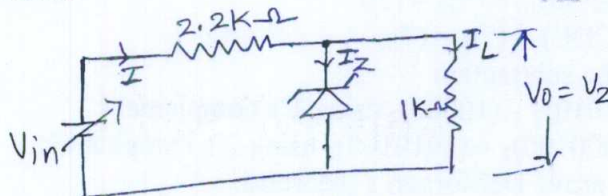

$$V_z = 6.1V, I_{z_{min}} = 2.5mA, I_{z_{max}} = 25mA, r_z = 0\Omega.$$

(04 Marks)

- c. Sketch the transistor input and output characteristics of CE configuration and briefly explain the three regions of operation. (06 Marks)

OR

- 2 a. With circuit diagram, explain the operation of center-tapped full-wave rectifier. Draw input and output waveforms. (06 Marks)
- b. Explain how zener diode can be used as voltage regulator. (05 Marks)
- c. Derive the relationship between  $\alpha$  and  $\beta$ . Find the values of  $\beta$ ,  $\alpha$  and  $I_E$  for a transistor has  $I_B = 100\mu A$  and  $I_C = 2mA$ . (05 Marks)


### Module-2

- 3 a. With neat circuit diagram, explain the operation of voltage divider bias circuit with necessary equations. (06 Marks)
- b. Draw the circuit of op-amp integrator. Derive the expression for output voltage. (06 Marks)
- c. Calculate the o/p voltage of a three input inverting summing amplifier, given  $R_1 = 200K\Omega$ ,  $R_2 = 250K\Omega$ ,  $R_3 = 500K\Omega$ ,  $R_f = 1M\Omega$ ,  $V_1 = -2V$ ,  $V_2 = -1V$  and  $V_3 = +3V$ . (04 Marks)

OR

- 4 a. For the circuit shown in Fig.Q.4(a) find the Q-point values and draw DC-load line, where  $V_{BE} = 0.7V$  and  $\beta = 50$ . (06 Marks)

Fig.Q.4(a)

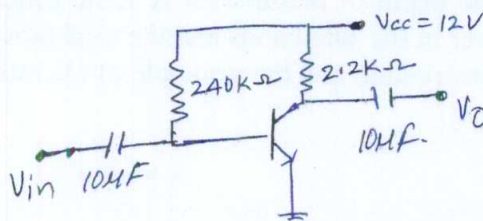

- b. Draw the circuit of non-inverting op-amp. Derive the expression for the voltage gain. (05 Marks)
- c. Define the following terms with respect to op-amp: i) slew rate; ii) CMRR; iii) PSRR. (05 Marks)

Module-3

- 5 a. Convert:
- i)  $(526.44)_8 = (?)_2 = (?)_{10}$
  - ii)  $(48350)_{10} = (?)_{16} = (?)_8$  (04 Marks)
- b. Subtract the following using 2's complement method:
- i)  $101011_{(2)}$  from  $111001_{(2)}$
  - ii)  $111001_{(2)}$  from  $101011_{(2)}$  (04 Marks)
- c. Simplify the following expression and realize using basic gates:  
 $Y = A(\overline{ABC} + \overline{A}BC)$ . (04 Marks)
- d. Realize half adder using NAND gates only. (04 Marks)

OR

- 6 a. Convert:
- i)  $(342.56)_{10} = (?)_2 = (?)_8$
  - ii)  $(BCDE) = (?)_2 = (?)_8$  (04 Marks)
- b. Perform the subtraction
- i)  $(11010)_2 - (10000)_2$  using 1's complement.
  - ii)  $(1000100)_2 - (1010100)_2$  using 2's complement. (04 Marks)
- c. State and prove DeMorgan's theorems. (04 Marks)
- d. Write the symbol, truth table and final expression for NAND and Ex – OR gate (For two I/PS). (04 Marks)

Module-4

- 7 a. With diagram and truth table explain NAND gate latch. (05 Marks)
- b. With diagram and truth table explain clocked R-S flip-flop. (05 Marks)
- c. Explain the architecture of 8051 microcontroller. (06 Marks)

OR

- 8 a. What is flip-flop? Explain the operation of NOR gate latch using its truth table. (08 Marks)
- b. With block diagram, explain microcontroller based stepper motor control system. (08 Marks)

Module-5

- 9 a. With the help of block diagram, explain communication system. (06 Marks)
- b. With circuit diagram explain the process of AM demodulation. (05 Marks)
- c. Explain the principle of operation of piezoelectric transducer. (05 Marks)

OR

- 10 a. Why modulation is necessary in communication system? List the different types of modulation schemes. (05 Marks)
- b. A carrier of 1MHz, with 400 W of its power is amplitude modulated with a sinusoidal signal of 2500Hz. The depth of modulation is 75%. Calculate the sideband frequencies, the band width, the power in the side bands and the total power in the modulated wave. (05 Marks)
- c. Explain the construction and the principle of operation of LVDT. (06 Marks)

\* \* \* \* \*

# CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

15ELN15/25

First/Second Semester B.E. Degree Examination, June/July 2017

## Basic Electronics

Time: 3 hrs.

Max. Marks: 80

*Note: Answer FIVE full questions, choosing one full question from each module.*

### Module-1

- 1 a. Explain briefly the PN junction diode characteristics. (06 Marks)
- b. Explain Zener diode voltage regulator circuit with no load and with load. (06 Marks)
- c. Derive the relationship between  $\alpha$  and  $\beta$ . Calculate the value of  $I_c$  for a transistor that has  $\alpha = 0.98$  and  $I_b = 200 \mu A$ . (04 Marks)

OR

- 2 a. Explain briefly the common emitter circuit and sketch the input and output characteristics. Also explain operating regions by indicating them on characteristics curve. (06 Marks)
- b. With a neat circuit diagram and waveforms, explain the working of a half-wave rectifier. (06 Marks)
- c. Explain briefly capacitor filter circuit. (04 Marks)

### Module-2

- 3 a. What is a DC load line? Explain the voltage divider bias circuit. (08 Marks)
- b. Mention and explain the characteristics of ideal operational amplifier. (04 Marks)
- c. Derive the expression of integrator with circuit diagram. (04 Marks)

OR

- 4 a. With neat circuit and necessary equations, explain the voltage follower. (06 Marks)
- b. Explain the base bias circuit. (04 Marks)
- c. Explain briefly inverting and non-inverting operational amplifiers. (06 Marks)

### Module-3

- 5 a. State and prove De-Morgan's theorem with truth table. (06 Marks)
- b. Explain the basic gates AND, OR and NOT gates with truth tables. (06 Marks)
- c. Explain the half-adder circuit. (04 Marks)

OR

- 6 a. Explain the full-adder circuit. (06 Marks)
- b. Simplify the given Boolean equation  $Y = (A + \bar{B})(CD + E)$  and realize using NAND gates only. (04 Marks)
- c. Convert the following:
  - i)  $(49.5)_{10} = ( \quad ? \quad )_{16}$
  - ii)  $(1062.403)_8 = ( \quad ? \quad )_{10}$
  - iii)  $(642.71)_8 = ( \quad ? \quad )_2$
 (06 Marks)

### Module-4

- 7 a. What is R-S flip-flop? Explain its circuit diagram, logic symbol and truth table. (08 Marks)
- b. Explain the architecture of 8051 microcontroller in detail. (08 Marks)

OR

- 8 a. Explain the gated R-S flip-flop and clocked R-S flip-flop. (08 Marks)  
b. With the help of block diagram, explain the micro-controller based stepper motor control system. (08 Marks)

**Module-5**

- 9 a. Explain the construction of LVDT and its operation. (06 Marks)  
b. Explain the frequency modulation with neat waveforms. (06 Marks)  
c. Explain with diagram the AM detection (demodulation). (04 Marks)

OR

- 10 a. Explain the piezoelectric transducer and photoelectric transducer. (06 Marks)  
b. Explain with block diagram elements of communication system. (06 Marks)  
c. Compare AM and FM modulation. (04 Marks)

\* \* \* \* \*

# CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

15ELN15

## First Semester B.E. Degree Examination, Dec.2015/Jan.2016 Basic Electronics


Time: 3 hrs.

Max. Marks: 80

**Note:** Answer any FIVE full questions, choosing one full question from each module.
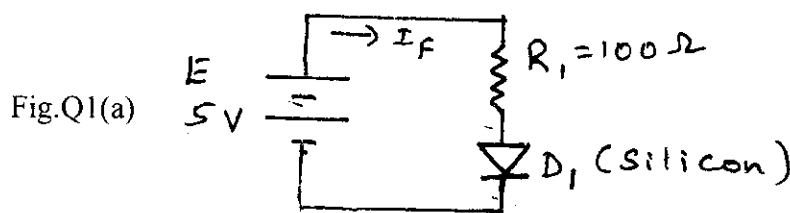
### Module-1

- 1 a. For the circuit shown in fig.Q1(a) draw the DC load line and locate Q – pt. (04 Marks)



- b. What is the need for capacitor filter? For a Half – Wave Rectifier, explain the operation of C – filter. (06 Marks)
- c. Considering npn transistor in common emitter configuration, explain how it acts as voltage amplifier. (06 Marks)

OR

- 2 a. Explain the working of a Bridge Full – Wave Rectifier, with a neat circuit diagram and waveforms. (06 Marks)
- b. Discuss the load and line regulation using zener diode with neat circuit diagram and appropriate expressions. (06 Marks)
- c. Calculate the values of  $I_C$  and  $I_E$  for a BJT with  $\alpha_{dc} = 0.97$  and  $I_B = 50 \mu A$ . Determine  $\beta_{dc}$ . (04 Marks)

### Module-2

- 3 a. Precisely analyse the circuit of voltage divider bias and hence determine the  $V_C$  and  $V_{CE}$ . Mention the advantages of voltage divider bias. (10 Marks)
- b. Derive an equation for output voltage for a non – inverting Op – amp. Find the gain of amplifier if  $R_F = 10K\Omega$  and  $R_1 = 1K\Omega$ . (06 Marks)

OR

- 4 a. A base bias circuit with a 12V supply uses a transistor with  $h_{FE} = 70$ . Design the circuit so that  $I_C = 2mA$  and  $V_{CE} = 9V$  (Assume  $R_E = 0$ ). (06 Marks)
- b. Explain the working of Op – amp as integrator. (05 Marks)
- c. Derive the expression of 3 input summing amplifiers. (05 Marks)

### Module-3

- 5 a. Convert the following : i)  $172.625_{(10)} = ( )_2$  ii)  $(ABCD.72)_{16} = ( )_8$   
iii)  $(10111101.0101)_2 = ( )_{10}$ . (06 Marks)
- b. Perform the following operations using 1's and 2's complement technique  
i)  $(56)_{10} - (79)_{10}$  ii)  $(23)_{10} - (18)_{10}$ . (06 Marks)
- c. State and prove de Morgan's theorem using truth table for 2 variables. (04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator, will be treated as malpractice.

OR

- 6 a. Explain full adder circuit with truth table. Realise the circuit for sum and carry using basic gates. Also write the diagram showing FA using two half adders. (06 Marks)
- b. Simplify and realize the following expressions using only NAND and NOR.  
 i)  $Y = (A + \bar{B})(B + C)(\bar{C} + \bar{B})$  ii)  $Y = AB + AC + BD + CD.$  (10 Marks)

**Module-4**

- 7 a. Explain the operation of NOR Latch with symbol, circuit and truth table. (06 Marks)
- b. With a neat block diagram, explain the architecture of 8051 microcontroller. (10 Marks)

OR

- 8 a. How is Flip – Flop different from a Latch? Explain the gated RS Flip – Flop with symbol, circuit and truth table. (08 Marks)
- b. Interface stepper motor to 8051 microcontroller with a neat block diagram. Explain its working principle. (08 Marks)

**Module-5**

- 9 a. Explain Amplitude Modulation with relevant waveforms. Derive the equation for instantaneous value of modulated signal in volts and define modulation index. (08 Marks)
- b. Define the term transducer. Mention any four characteristics a transducer should possess. (02 Marks)
- c. Briefly explain the working of thermistor. Mention its applications. (06 Marks)

OR

- 10 a. Explain the frequency modulation with necessary waveforms. Bring out the difference between AM and FM. (08 Marks)
- b. Explain construction and the principle of operation of LVDT. (08 Marks)

\* \* \* \* \*